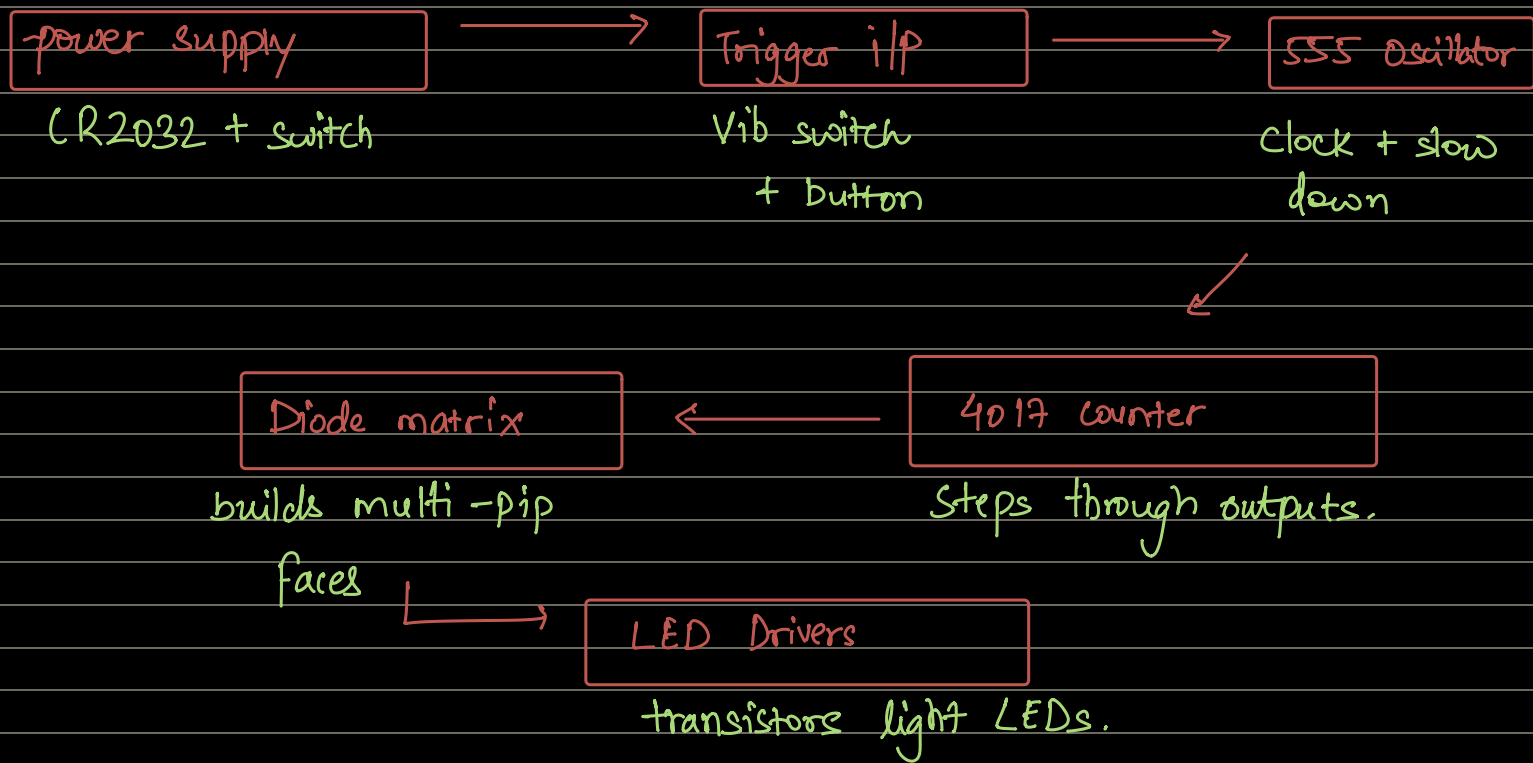


Electronic Dice Project

Roadmap




calculations The slow down effect

τ → time const. ⇒ voltage in cap to drop to about 37% of its original value.

$$\tau = R \times C \rightarrow \therefore C = 1\mu\text{f}$$


we fancy about 1.5 secs.

Connections

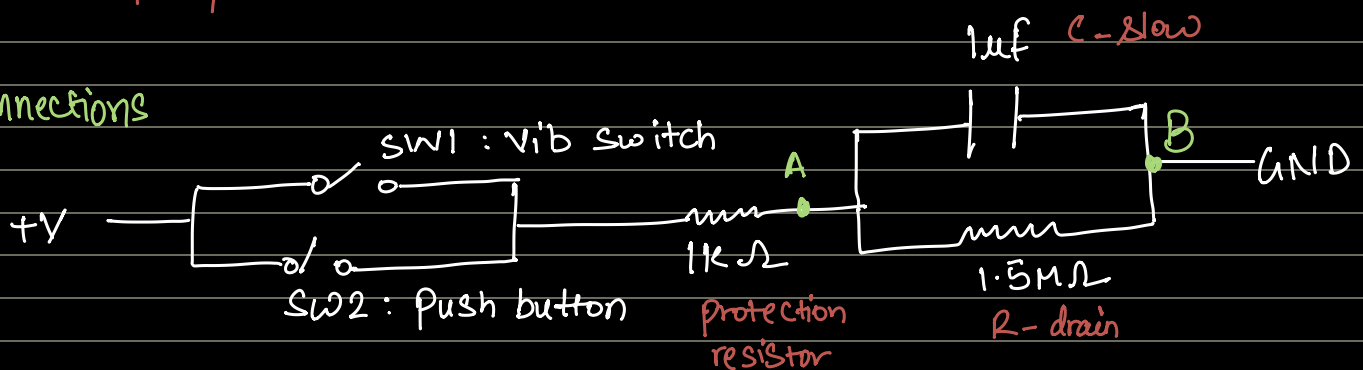


* Node A → connect to pwr pin of 555 timer.


555 Oscillator IC.

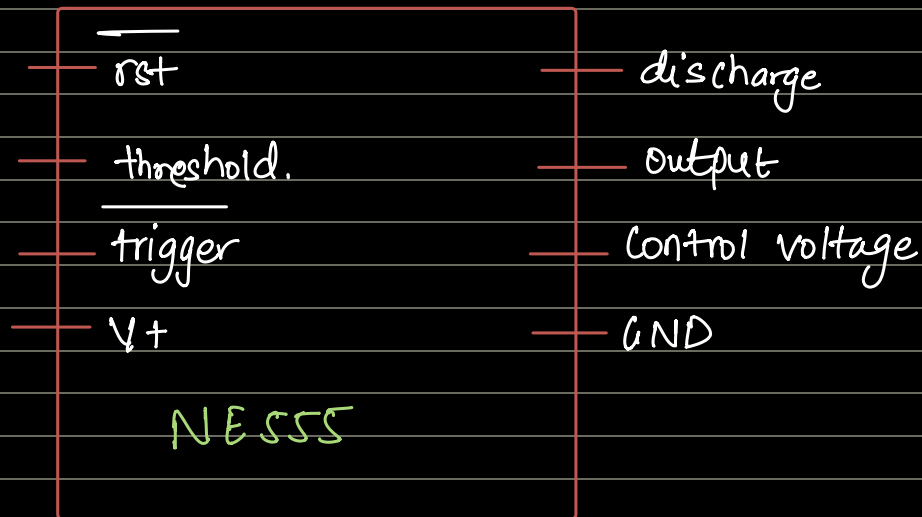

connections.

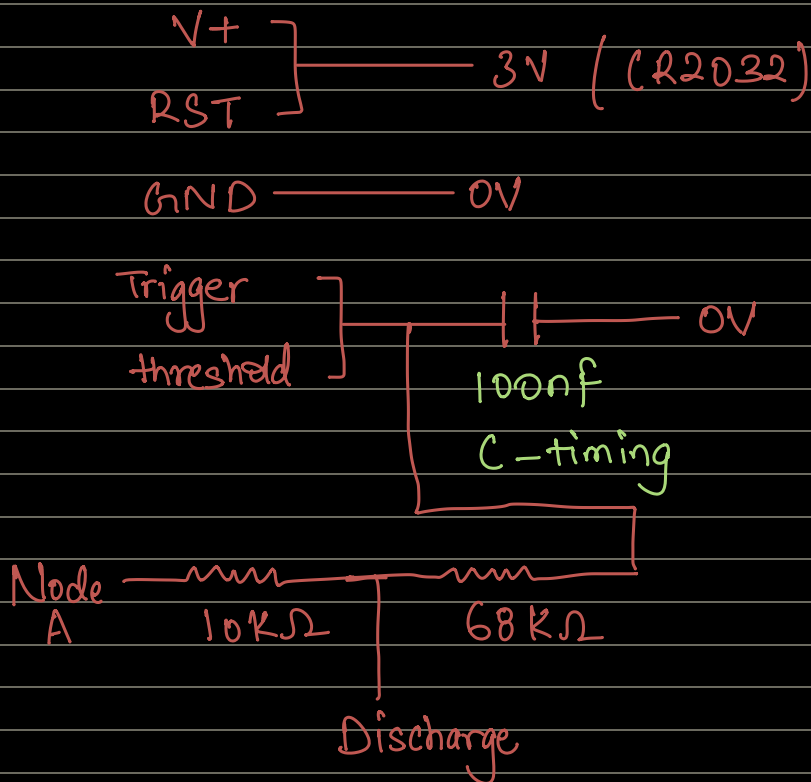


CD 4017 Decade counter

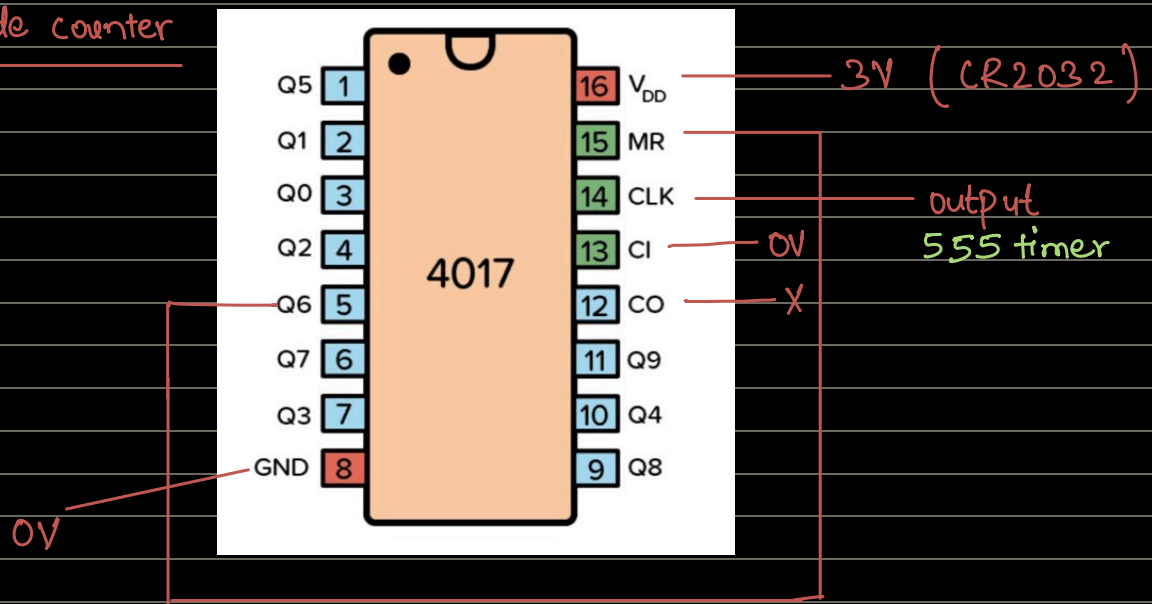


Q6 → Reset ∴ only 6 states exist.

Display

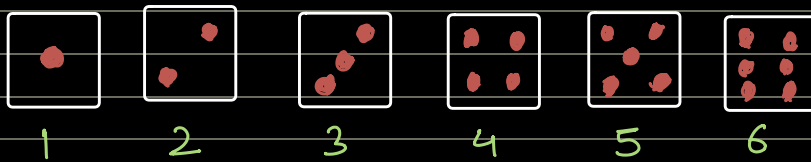

Split it into unique parts.

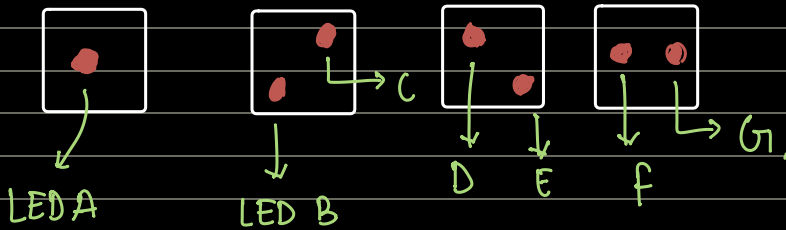

Part 1 Part 2 Part 3 Part 4.

Truth table

→ * Default ON!

Roll	part 1	part 2	part 3	part 4
Q0 1	1	0	0	0
Q1 2	0	1	0	0
Q2 3	1	1	0	0
Q3 4	0	1	1	0
Q4 5	1	1	1	0
Q5 6	0	1	1	1

* because part 2 ON for 5 states $\rightarrow \therefore$ Default ON.

